
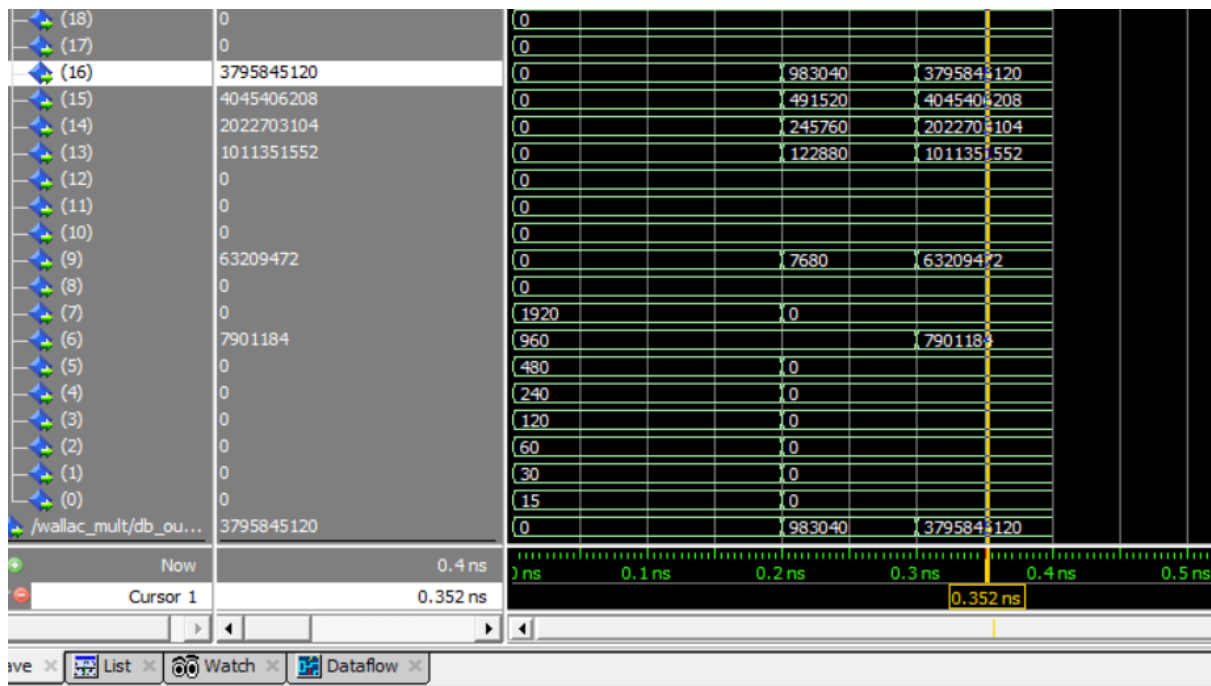


Results Of Wallace Multiplier Simulations


Partial Product Generation

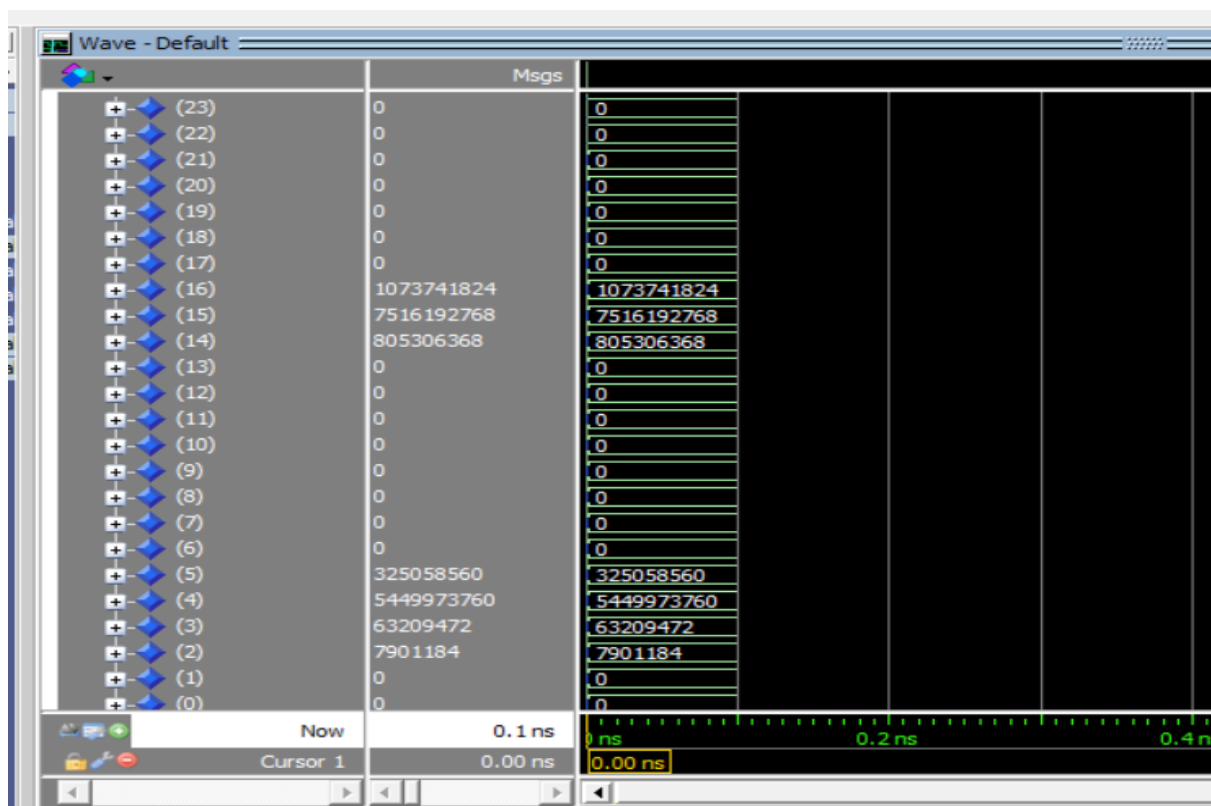

Layer 1 reduction




Layer 2 Reduction

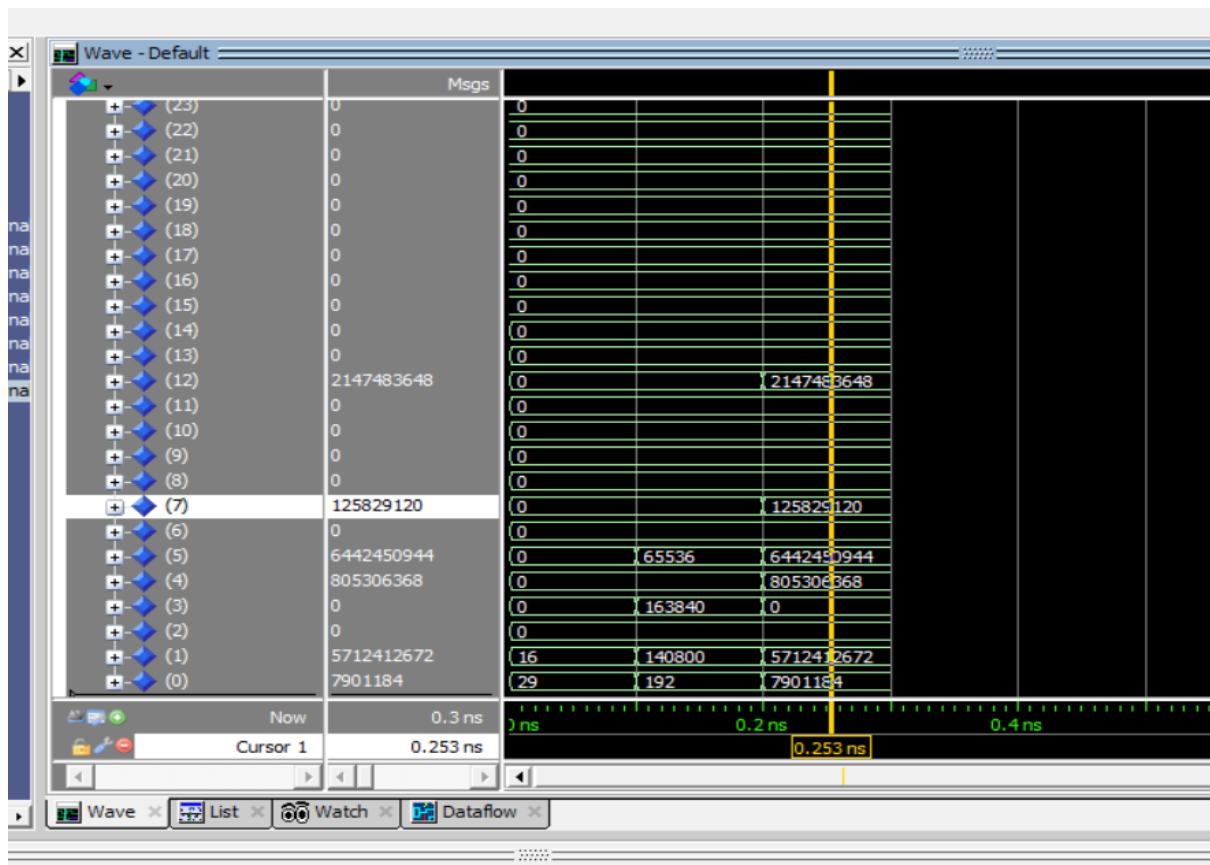


is not in bounds of subtype NATURAL.


Layer 3 Reduction

 


Layer 4 Reduction

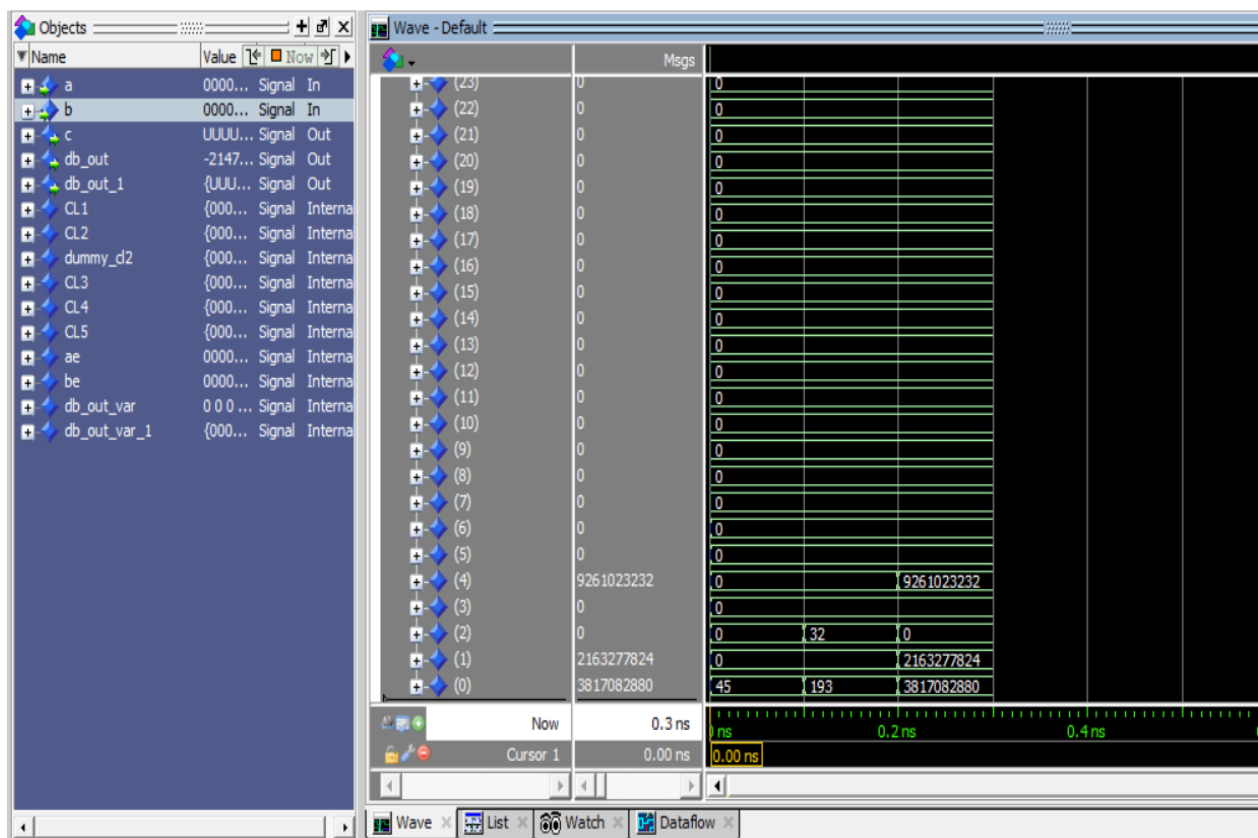


Layer 5 Reduction

 


Layer 6 Reduction

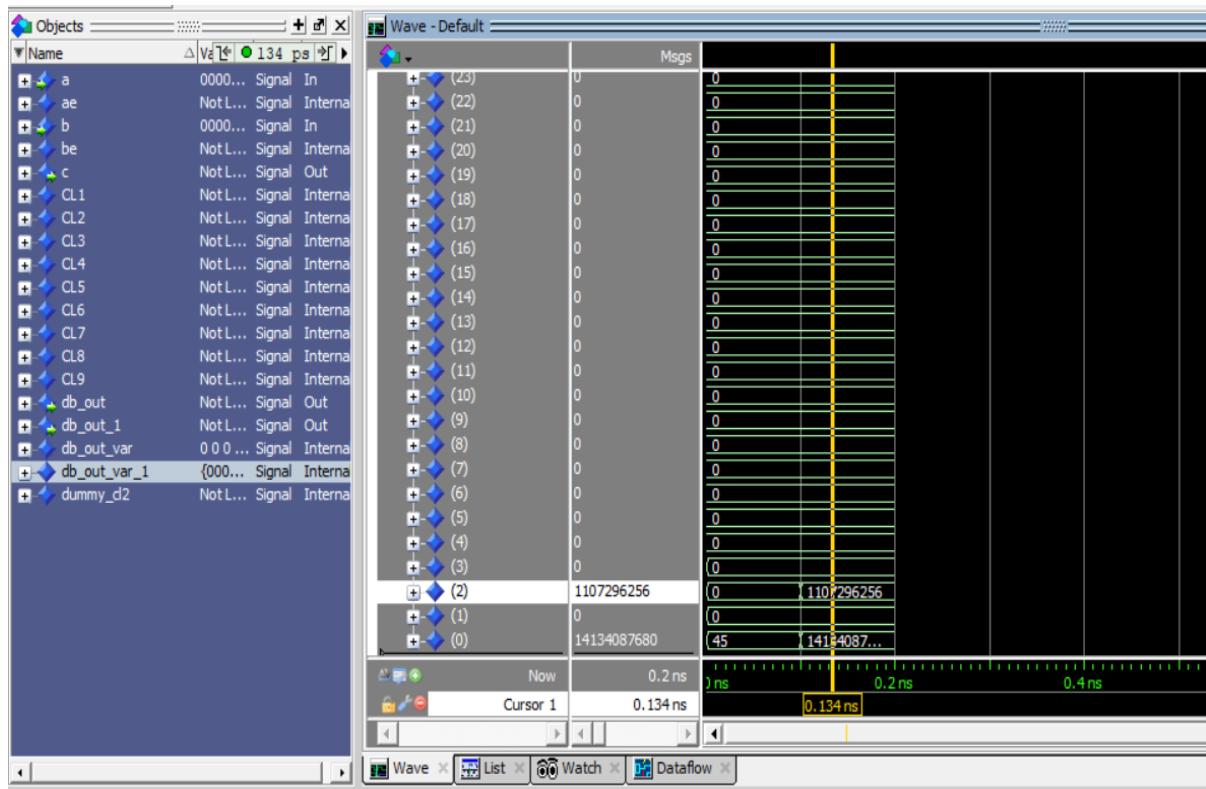


Layer 7 Reduction

 

Layer 8 Reduction

 

Final Result With Adder

 

Pipelined Version of Wallace Multiplier

Code Modification:

```

process (clk) begin
  if (clk'event and clk = '1') then
    CL1_latched <= CL1 ;
    CL2_latched <= CL2 ;
    CL3_latched <= CL3 ;
    CL4_latched <= CL4 ;
    CL5_latched <= CL5 ;
    CL6_latched <= CL6 ;
    CL7_latched <= CL7 ;
    CL8_latched <= CL8 ;
    CL9_latched <= CL9 ;
    ae(31 downto 0) <= a;
    be(31 downto 0) <= b;
  end if ;
end process ;

```

Test Bench:

```

entity wallac_mult_tb is
end entity ;

architecture behave of wallac_mult_tb is

  signal a, b: std_logic_vector(31 downto 0) := (others => '0') ;

  signal x : std_logic_vector(63 downto 0) ;

  signal clk : std_logic := '0' ;
  signal enable_clk : std_logic := '1' ;

begin
  dut: wallac_mult port map (a => a, b=> b, c => x, clk => clk) ;

  clk <= (not clk ) and enable_clk after 10 ps ;

  process (clk) begin
    if (clk'event and clk = '1') then
      a <= std_logic_vector(to_unsigned((to_integer(unsigned(a))+101), 32)) ;
      b <= std_logic_vector(to_unsigned((to_integer(unsigned(b))+110), 32)) ;
    end if ;
    if (to_integer(unsigned(a)) > 10000) then
      enable_clk <= '0' ;
    else
      enable_clk <= '1' ;
    end if ;
  end process ;
end architecture ;

```

Result:

